

Popular Electronics*

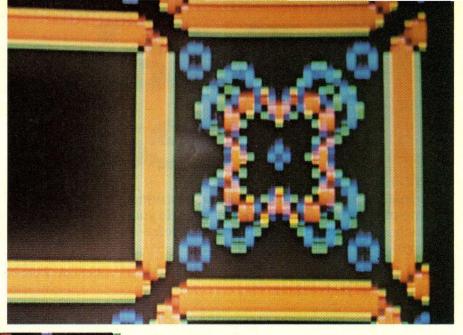BY TERRY WALKER, ROGER MELEN, HARRY GARLAND ED HALL



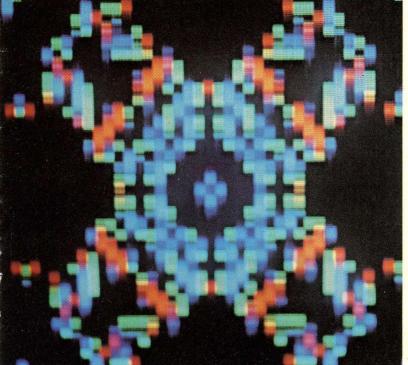


BUILD THE TV DAZZLER

Unique computer accessory provides alphanumerics and graphics in full color.

HE TV DAZZLER provides versatile electronic coupling between a small home computer and a color TV set. It can be used to generate action games, animated displays, educational learning drills, graphs, even light shows-all in full color! The Dazzler is designed to plug directly into the Altair 8800 computer (POPULAR ELECTRONICS, Jan. 1975); however, since it uses direct memory access (DMA) to scan the computer memory, it can easily be used with many other computers. If a Teletypewriter is your only communications link with your computer, here is a chance to build this new concept in computer peripherals at less than the



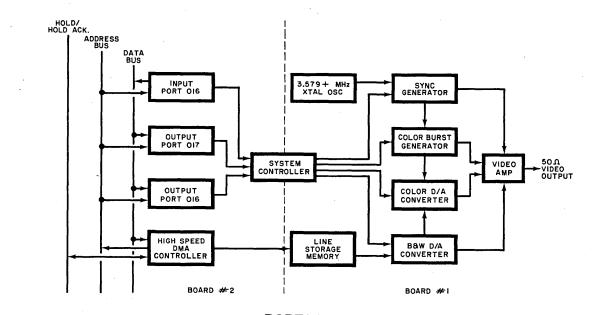

PARTS LIST

- C1 through C9,C18 through C25-0.1-µF disc ceramic capacitor
- C10,C11,C26,C27-47-µF, 20-volt tantalum capacitor
- C12-330-pF disc capacitor
- C13-680-pF disc capacitor
- C14,C15,C16-470-pF disc capacitor
- C17-9-35-pF variable capacitor
- D1-1N914 silicon diode
- D2-1N5242B, 12-volt zener diode
- IC1,IC37—LM340-5.0, 5-volt regulator
- IC2,IC16,IC17,IC18—SN7410N triple 3-input positive NAND gate
- IC3,IC10—SN7473N dual J-K masterslave flip-flop
- IC4,IC21,IC56—SN7432N quad 2-input OR gate
- IC5,IC30—SN7430N 8-input positive NAND gate
- IC6,IC23,IC42,IC43—SN7474N dual D-type edge-triggered flip-flop
- IC7,IC19,IC35,IC40,IC48—SN7404N hex inverter
- IC8,IC22,IC25,IC39,IC51—SN7408N quadruple 2-input positive AND gate IC9,IC14,IC15,IC28—SN7400N quad-
- ruple 2-input NAND gate IC11,IC12,IC31,IC32,IC49,IC50,IC52— SN7493N 4-bit binary counter
- IC13,IC27,IC33,IC45—SN74157N quadruple 2-input data selector
- IC20,IC29—SN7420N dual 4-input positive NAND gate

- IC24—F3342DC 64 x 4 MOS shift register (Fairchild)
- IC26—SN74151N 8-line to 1-line data selector
- IC34,IC46,IC54—SN74175N quadruple D-type edge-triggered flip-flop
- IC36,IC53,IC55,IC61,IC63,IC64-
- SN7475N quadruple bistable latch IC38—SN7402N quadruple 2-input positive OR gate
- IC41—SN74LS10N triple 3-input positive NAND gate
- IC44—SN74LS30N 8-input positive NAND gate
- IC47—SN74LS08N quadruple 2-input positive AND gate
- IC57—SN7495N 4-bit universal shift register
- IC58,IC59,IC65,IC72,IC73—SN74LSO4N register
- IC60,IC62—SN7483N 4-bit binary full adder
- IC66,IC67,IC74-SN7405N hex inverter with open collector
- IC68,IC69,IC70,IC71—SN74367 hex tristate buffer
- Q1-2N3904 transistor
- Q2,Q3-2N3906 transistor
- Following resistors are 5%, 1/4 watt:
- R1-150 ohms
- R2,R3-1000 ohms
- R4-470 ohms
- R5,R6,R7,R29-1200 ohms

R9—18,000 ohms R11—7500 ohms R12—15,000 ohms R13—62,000 ohms

R13-62,000 onms

R8,R10-9100 ohms

- R14—30,000 ohms
- R15 through R20-13,000 ohms
- R21-820 ohms
- R22-1500 ohms R23-330 ohms
- R24—220 ohms
- R25—51 ohms
- R26-100 ohms
- R27-22 ohms
- R28-680 ohms
- R30,R31,R32-500-ohm trimmer potentiometers
- XTAL-3.579545 MHz
- Misc.—IC sockets (74), heat sinks (2), mounting hardware
- Note: The following are available from Cromemco, 1 First St., Los Altos, CA 94022: complete set of parts less IC sockets at \$195; with IC sockets at \$215, assembled and tested Dazzler for \$350. California residents please include sales tax. Prices include postage for orders shipped within the U.S. Partial kits are not available. The schematic and foil patterns are available *free of charge* by sending a stamped (for 3 oz.) self-addressed 9" by 12" envelope to Cromemco, 1 First St., Los Altos, CA. 94022.

Fig. 1. Board 1 of the Dazzler contains an NTSC color TV signal generator with output through a 50-ohm line. Board 2 communicates with the computer and modulates the TV signal.

cost of a black-and-white terminal; and you do not need an RS-232 interface. The Dazzler can be built for less than \$200.

If you use your computer for business or accounting, the Dazzler can display multi-colored graphs of stored data. It can also be used to display a picture produced by the Cyclops solid-state camera (POPULAR ELEC-TRONICS, February 1975). With the Cyclops picture either processed or unprocessed, the system can be used for security purposes, pattern recognition tests, and measurement and control of processes. **How It Works.** A block diagram of the Dazzler is shown in Fig. 1. Most of the components on board #1 are used to generate a conventional NTSC (National Television Standards Committee) color video signal. The circuit is terminated in a 50-ohm, 1-volt output. This signal can be used to drive the

37

D7 D6 D5 D4 D3 D2 D1 D0 DN/OFF A15 A14 A13 A12 A11 A10 A9 SE1	OUTPUT PORT 016					
ON/OFF AI5 AI4 AI3 AI2 AII AI0 A9 SEI	D7					
ON/OFF AI5 AI4 AI3 AI2 AII AI0 A9 SEI SW	ON/OFF					

starting address of picture in MEMORY video amplifier of a color set or to modulate a class-1 TV device connected to the set's antenna terminals (using a locally unoccupied channel).

The components on board #2 are used to communicate with the computer, with a high-speed DMA controller

Output Port 017

Fig. 2. Configuration of the data bits at output port 016.

as the basis. The controller issues a "hold" command when it is ready to access the computer memory. When the computer is ready, it issues a "hold acknowledge" command and the DMA begins operation.

Communication between the Daz-

D7 - not used	
1 Resolution X4. Color and inte	ensity set by D4 through D0.
D6 $\begin{cases} 1 \text{ Resolution X4. Color and integral} \\ 0 \text{ Normal resolution (32 x 32 for a data)} \end{cases}$	r 512 bytes,64 x 64 for 2K
bytes). Color and intensity a	set by 4-bit words in
computer memory.	
1 Picture in 2K bytes of memory	
D5 D5 D5 1 Picture in 2K bytes of memory 0 Picture in 512 bytes of memory	y
1 Color picture	
D4 { 1 Color picture 0 Black-and-white picture	
D3 { 1 High intensity color }	Most significant hit of
0 Low intensity color	4-bit B/W intensity
(1 Blue	
D2 { 1 Blue O No blue	*
(1 Green	
D1 { Green 0 No green	*
(1 Red	
DO { 1 Red 0 No red	Least significant bit

Fig. 3. The states of seven data bits at output port 017 determine resolution of TV picture and either chroma or monochrome parameters.

Memory Location	Memory Contents	Comments
000 000	076	Move immediate into
000 001	200	the accumulator.
000 002	323	Output to port
000 003	016	number 016.
000 004	333	Input
000 005	377	from sense switches.
000 006	323	Output to port
000 007	017	number 017.
000 010	303	Jump to
000 011	000	memory location 000
000 012	000	000.

Fig. 4. A test program to be used on the TV Dazzler.

zler and the host computer is through output ports 016 and 017 and input port 016. One bit of output port 016 is used to turn the Dazzler on and off, and the remaining seven bits are used to set the starting address of the picture in the computer memory. The organization of output port 016 is shown in Fig. 2.

Output port 017, whose organization is shown in Fig. 3, is used to set the format of the TV picture. Note that bit D7 is not used. Bit D6 is used to set normal resolution (32 x 32 for 512 bytes or 64 x 64 for 2K bytes) or 4X resolution (64 x 64 for 512 bytes or 128 x 128 for 2K bytes). Bit D5 sets the amount of computer memory, starting at the location given to output port 016, allocated to the picture. When 512 bytes are selected, the computer memory must have an access time of at least one microsecond. When 2K bytes are used, the memory must have an access time of at least 500 nanoseconds.

Bit D4 is used to select either a black-and-white or color display. In the 4X resolution mode (D6 at a 1), bits D3 to D0 are used to set the color of the display when in the color mode or the intensity when D4 is in the blackand-white mode. Bits D3 to D0 are not used in the normal resolution mode.

Only two bits of input port 016 are used. When bit D7 is a 1 (high), it indicates that the Dazzler is enabled (bit D7 of output port 016 actually performs the enabling), while bit D6 goes low to indicate an end of frame. This latter bit is useful when changing frames in rapid succession.

To generate a TV picture with the Dazzler, the information that the Dazzler reads from the computer memory must be properly formatted. In the 4X resolution (output port 017, bit D6 high), each point on the TV screen is controlled by just one bit in the computer memory. This bit turns its corresponding point in the picture on or off. The color or intensity of that frame of the picture is set by bits D3 through D0 of the control word at output port 017. To get full color in the 4X mode, multiple frames of different colors must be interleaved.

In the normal resolution mode (output port 017, bit D6 low), the color and intensity of each point on the screen is controlled by a four-bit "nybble" in the computer memory. Two points of the picture are thus encoded in each byte of the computer memory. For this reason, a 64 x 64 picture requires 2K of

POPULAR ELECTRONICS

38

THE GAME OF LIFE


One of the most fascinating uses of the Dazzler is in playing what is known as "The Game of Life." (See *Scientific American*, October 1970, p 120; February 1971, p 112; April 1971, p 116.) The game is started by entering the program shown below. (A paper tape of the program is available for \$15 from Cromemco, 1 First St., Los Altos, CA 94022.) Then a colony of cells is entered to appear on the TV screen on a 64 x 64 grid.

Each cell in the colony has eight possible neighbors, as shown at right. The evolution of the colony proceeds according to a fixed set of rules invented by John Conway at the University of Cambridge. Every cell with two or three neighbors will survive to the next generation. Every cell with four or more neighbors dies from over-population. Every cell with one neighbor or no neighbors dies from isolation. Every cell with exactly three neighbors is a birth cell—a new cell is born here in the subsequent generation.

In the Dazzler version of The Game of Life, blue represents life; birth generates a green cell; and death is shown in red. There are many surprises to be found in the game. Some colonies survive and prosper; others reach a stable state—neither growing nor lessening. Other colonies fade from existence. Some colonies, known as "gliders" sail across the screen and can be devoured by other colonies in the process.

The full-color illustrations on the first page of this article are actual photos of a TV screen several generations into a Life program.

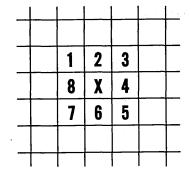The initial colony of cells is drawn on the TV screen using ASCII keyboard inputs as controls. Control A deposits a cell of life on the screen. Controls N, O, P, and H step the cursor up, down, right, and left, respectively. Once the initial colony is complete, Control D is initiated to start the game.



Each cell has 8 possible neighbors.

Program for Game of Life is below. DAZZLE-LIFE PRØGRAM (LØADS BEGINNING 000 000, RUNS FRØM 000 000)

ØCTAL·LISTING (000 000 = 061, 000 001 = 000, 000 002 = 010 ETC.)

FEBRUARY 1976

memory storage. The lowest order (D0) bit determines if the display is red, D1 is green, D2 is blue, and D3 determines either a high- or low-intensity color. In black and white, these four bits are used to determine one of 16 shades of gray.

Construction. The Dazzler consists of two adjoining pc boards that plug directly into the Altair-8800 bus connectors. The video output is taken from a pad on board #1. The schematics, etching and drilling guide and component placement diagram for the boards are too large for reproduction here. They can be obtained FREE by sending a stamped, self-addressed 9" by 12" envelope to Cromemco, 1 First St., Los Altos, CA 94022. (These items are also included with each kit as mentioned in the Parts List.)

In assembling the pc boards, note that all components are mounted on one side of the board, with all soldering on the opposite side. The sides to be soldered are those on which the foil marking can be properly read. Platedthrough holes assure contact on the component side. If desired, sockets can be used for mounting the IC's. When soldering, use a low-wattage iron and fine solder. Inspect your work to make sure you have no solder bridges.


Because portions of the Dazzler operate at very high frequencies, it is important that all components be mounted close to the pc board. Be sure to use components that meet the required specifications—some untested IC's may not have the required switching speeds.

There are 36 IC's on board 1, plus the color crystal oscillator, and associated passive components. A heat sink is used for *IC1*, the 5-volt regulator on board #1. When mounting the color-burst crystal, use a small length of wire soldered from the metal case of the crystal to the ground foil immediately above the case. This reduces noise pickup.


One of the center dual in-line positions in the bottom row of board #1 is used for board-to-board interconnections rather than an IC.

There are 37 IC's on board #2. One dual in-line position is left open for interconnections. To connect the two boards, use sixteen 8" lengths of insulated wire (or a 16-conductor flat cable).

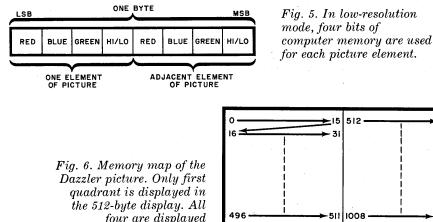The two boards are attached using %" spacers at each corner hole, with



four are displayed in 2K-byte picture.

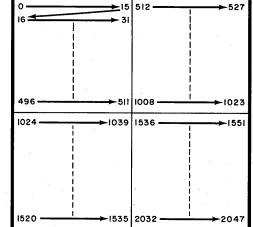


the component side of one facing the soldered side of the other. The two are separated by exactly the same distance as two adjacent connectors on the Altair bus.


Check-Out. Check for solder bridges and proper component orientation. Facing the component side of a board, pin 1 of each IC should be at the lower left. Check the interconnections between the boards.

Turn off the power to the Altair and then insert the Dazzler into adjacent sockets on the bus line. Using a length of coaxial cable, connect the Dazzler video output (ground the coax braid to

the adjacent ground foil) to the video input and signal ground of your color TV receiver. The connection can usually be made at the input to the video amplifier, with a switch to select the normal input or the Dazzler input.

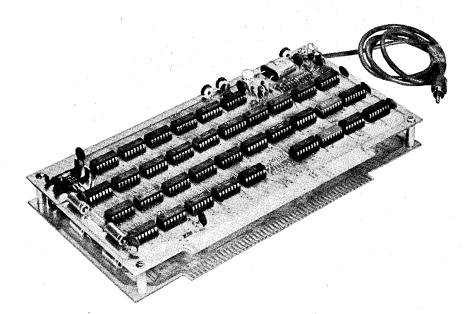Tune-Up. The Dazzler is activated and deactivated by software control. The simple program shown in Fig. 4 will turn the Dazzler on and display a picture that is stored starting at location zero in memory (D0 through D6 of output port 016 at zero). This short program also allows sense switch control of the word sent to output port 017. The sense switches are labelled



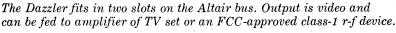

A8 through A15 on the front panel of the Altair.

Load from the program in Fig. 4 into the Altair from the front panel, examine zero and run the program beginning at location zero in memory. (Be sure all sense switches are down.)

With the color TV set operating and the Altair "running", raise sense switch A12 and note that a colorful quilt-like pattern appears on the screen. Potentiometer R30 (bias) on board 1 of the Dazzler acts as a horizontal hold control and should be adjusted to obtain a stable picture.

Raise sense switches A10 and A11, and adjust capacitor C17 on board #1 for the most saturated blue on the screen. Now put A10 down, raise A9, and adjust R32 for the most saturated green color. Finally, set A9 down, raise A8, and adjust R32 for the most saturated red color.

Dazzler Software. When writing programs for the Dazzler, it is important to remember that the TV picture is stored as a specially coded sequence in the computer memory. The Dazzler simply interprets this code to form the TV image.

Two different codes are used depending on whether the Dazzler is in the low-resolution or high-resolution mode. This is determined by the control word at output port 017. In the low-resolution mode, four bits of computer memory are used to code each element of the picture (Fig. 5). Either a 32 x 32 or 64 x 64 element picture can be displayed. The latter is organized as quadrants within the computer memory as shown in Fig. 6.

In the high-resolution mode, each bit of memory is used either to turn on

0 LSB	l	4	5
2	3	6	7 MSB

Fig. 7. In high-resolution mode, each memory byte is used to represent 8 picture elements.

(bit=1) or off (bit=0) a single memory element. The control word output to port 017 is used to set the picture color. Figure 7 shows how one byte of memory is divided up to control eight elements of the picture. In this mode, either a 64 x 64 element picture using 512 bytes or a 128 x 128 element picture using 2K bytes can be displayed on the screen. ۲

POPULAR ELECTRONICS